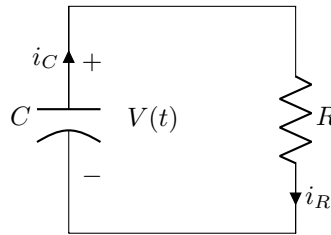


• 1st order circuits:


1. RC circuits:



Using KCL gives:

$$\begin{aligned} i_C + i_R &= 0 \\ \Rightarrow C \left(\frac{dV}{dt} \right) + \frac{V}{R} &= 0 \\ \therefore V(t) &= V_0 e^{-\frac{t}{RC}} \end{aligned}$$

2. RL circuits:

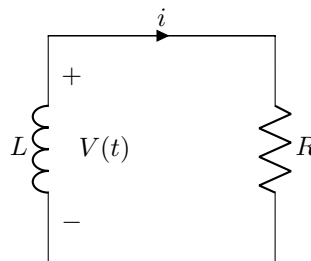


Using KVL gives:

$$\begin{aligned} Ri + L \left(\frac{di}{dt} \right) &= 0 \\ \therefore i(t) &= i_0 e^{-\frac{t}{\tau}} \end{aligned}$$

Where τ is the time constant of the circuit given by $\frac{L}{R}$

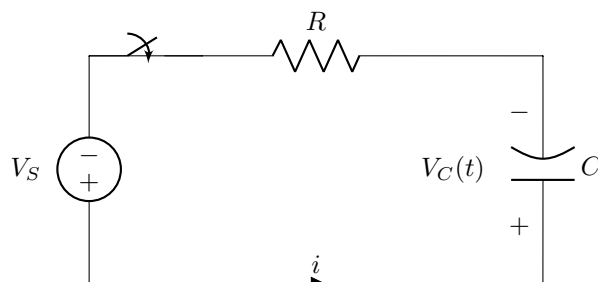3. Complete response:

Consider the following RC circuit with a source voltage V_S




Using KVL in the closed loop gives us the following:

$$\begin{aligned} V_S &= iR + V_C \\ \Rightarrow V_S &= RC \left(\frac{dV_C}{dt} \right) + V_C \\ \frac{dV_C}{dt} + \frac{V_C}{RC} &= \frac{V_S}{RC} \\ \therefore V_C(t) &= A e^{-\frac{t}{\tau}} + V_S \end{aligned}$$

The exponential term corresponds to the **natural response**, whereas the constant term V_S corresponds to the **forced response**. The value of the coefficient A is computed using the boundary conditions of the differential equation: $A = V_C(0) - V_S$

- **2nd order circuits:**

1. Natural response:

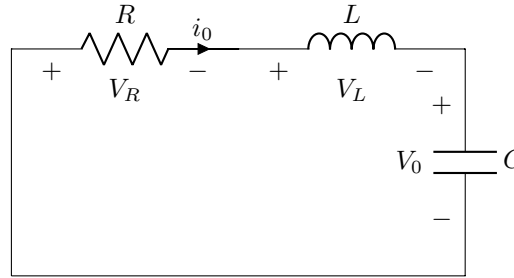

Applying KVL in the closed loop gives

$$\begin{aligned} V_R + V_L + V_0 &= 0 \\ \Rightarrow iR + L \left(\frac{di}{dt} \right) + V_0 &= 0 \\ \therefore L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} &= 0 \end{aligned}$$

Thus, we have the following characteristic differential equation: $s^2 + 2\alpha s + \omega_n^2 = 0$. The solutions of this equation take the form

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_n^2}$$

Here, $\alpha = \frac{R}{2L}$ and $\omega_n = \frac{1}{\sqrt{LC}}$. From this, we have 3 different cases that arise on account of the nature of the roots s_1, s_2 :

- (a) **Overdamped:** s_1, s_2 are **real and distinct**. Thus, $\alpha > \omega_n$. The natural solution takes the form $V_0(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
- (b) **Critically damped:** s_1, s_2 are **real**. Thus, $\alpha = \omega_n$. The natural solution takes the form $V_0(t) = A_1 e^{s t} + A_2 t e^{s t}$
- (c) **Under damped:** s_1, s_2 are **complex**. Thus $\alpha < \omega_n$. The roots $s_1, s_2 = -\alpha + j\omega_d$ where j is the quantity $\sqrt{-1}$ and $\omega_d = \sqrt{\omega_n^2 - \alpha^2}$. Hence, the natural solution of the the system is of the form $V_0(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$

2. **Forced response:** If we add a voltage source V_S to the previous circuit, it is easy to observe that by the superposition theorem, the quantity V_S simply gets added to the natural response solutions of the characteristic differential equations.

- **AC analysis:**

1. Impedance and admittance:

All the results (in particular, the solutions of 2nd order circuits) of DC circuit analysis carry forward here.

The **impedance** (Z) of the circuit elements is the AC analog resistance.

$$Z = \frac{V}{i} = R \text{ or } j\omega L \text{ or } \frac{1}{j\omega C}$$

Similarly, the AC analog of conductance is called **admittance** (Y)

$$Y = \frac{i}{V} = \frac{1}{R} \text{ or } \frac{1}{j\omega L} \text{ or } j\omega C$$

In both of these, j denotes the complex square root ($\sqrt{-1}$) and ω is the angular frequency of the voltage source.

2. Power:

Consider an AC voltage source with a time varying current $i(t)$ and a time varying voltage $V(t)$. The power due to this source is

$$\begin{aligned} p(t) &= v(t)i(t) = V_m \cos(\omega t + \varphi_1) I_m \sin(\omega t + \varphi_2) \\ &= \frac{1}{2} V_m I_m [\cos(\omega t + \varphi_1 + \omega t + \varphi_2) + \cos(\varphi_1 - \varphi_2)] \end{aligned}$$

Here, V_m and I_m denote the peak voltage and current respectively. From here, we calculate the average power to be

$$\langle p(t) \rangle = \frac{1}{2} V_m I_m \cos(\varphi_1 - \varphi_2)$$

Here, we define another quantity, the **RMS voltage** ($V_{\text{RMS}} = \frac{V_m}{\sqrt{2}}$). Using this, the average power is written as

$$\langle p(t) \rangle = V_{\text{RMS}} I_{\text{RMS}} \cos \theta$$

θ being the phase difference ($\varphi_1 - \varphi_2$). Note that φ_1 denotes the phase angle of voltage and φ_2 denotes the phase angle of current.

Also, the *RMS* voltage (and current) is computed by performing the following integral:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt}$$